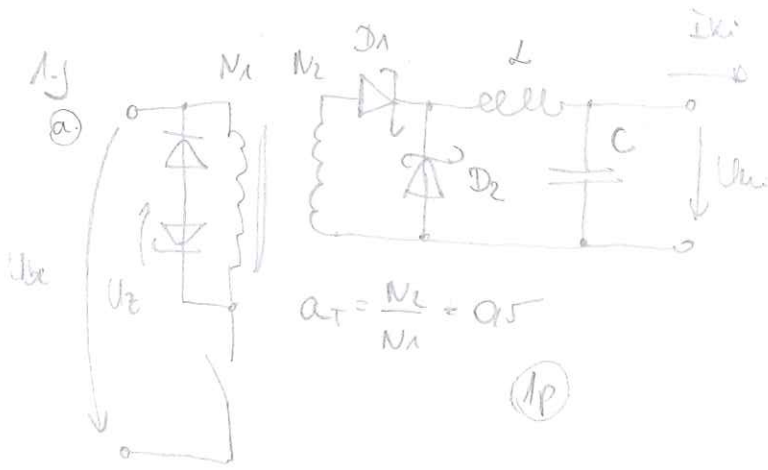


Táplóplágás 05.21:



- $U_{be} = 400V$
- $U_{ki} = 48V$
- $a_T = 0,5$
- $L_n = 5mH$
- $P_{ki} = 200W$
- $f = 50kHz$
- $\Delta I_L = 1A$
- $\Delta U_{ki} = 0,01$

(b)
$$U_{ki} = a_T \cdot U_{be} \cdot \frac{1}{1-d} = d \cdot \frac{U_{ki}}{a_T \cdot U_{be}} = \frac{48}{0,5 \cdot 400} = 0,24 \quad (1p)$$

(c)
$$\Delta I_L = \frac{a_T \cdot U_{be} - U_{ki}}{L} \cdot t_{be} = d \cdot \frac{L}{\Delta I_L} \geq \frac{a_T \cdot U_{be} - U_{ki}}{\Delta I_L} \cdot t_{be} = \frac{200 - 48}{1} \cdot 0,24 \cdot 20\mu s = 729,6\mu H \quad (1p)$$

$$\Delta U_{ki} = \frac{\Delta I_L \cdot T}{8C} \Rightarrow C \geq \frac{\Delta I_L \cdot T}{8 \Delta U_{ki}} = \frac{1 \cdot 20\mu s}{8 \cdot 0,01} = 250\mu F \quad (1p)$$

(d)
$$I_{crms} = \frac{\Delta I_L}{2\sqrt{3}} = \frac{1}{2\sqrt{3}} = 288mA @ 50kHz \quad (1p)$$

(e)
$$\hat{I}_{D1} = \hat{I}_{D2} = I_{AV} + \frac{\Delta I_L}{2} = I_{ki} + \frac{\Delta I_L}{2} = 5,5A \quad (1p)$$

$$\hat{U}_{D2} = a_T \cdot U_{be} = 200V \quad (1p)$$

$$\hat{U}_{D1} = U_2 \cdot a_T + U_{ki, max} = 200V \quad (1p)$$


(f)
$$U_{zmin} = U_{be} \cdot \frac{d}{1-d} = 400 \cdot \frac{0,24}{1-0,24} = 126,3V \quad (1p)$$

$$P_z = \frac{U_{ki}^2}{2 \cdot a_T^2 \cdot f} = \frac{48^2}{2 \cdot 0,5^2 \cdot 50 \cdot 10^3} = 18,4W \quad (1p)$$

(g)
$$U_{max} = U_{be} + U_2 = 400 + 126,3 = 526,3V \quad (1p)$$

$$I_{max} = \hat{I}_L \cdot a_T + \frac{U_{be}}{f \cdot L} = 5,5 \cdot 0,5 + \frac{400}{5 \cdot 10^{-3}} \cdot 0,24 \cdot 20\mu s = 3,134A \quad (1p)$$

$$| \leq 11p$$

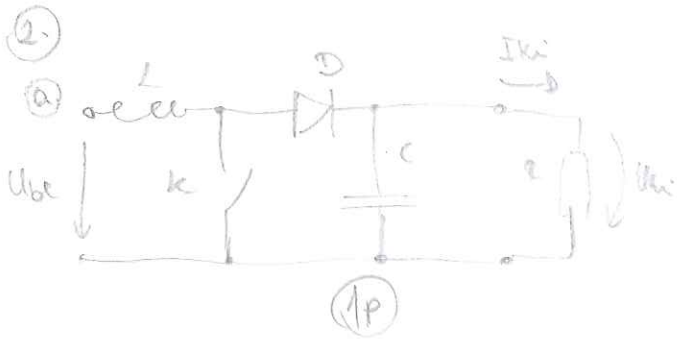

$U_{be} = 12V$
 $U_{ki} = 48V$
 $I_{ki} = 5A$
 $\Delta I_L = 5A$
 $\Delta U_{ki} = 0,01V$
 $f = 100kHz$

b.

$$d = 1 - \frac{U_{be}}{U_{ki}} = 1 - \frac{12}{48} = 0,75$$

$$t_{be} = d \cdot T = 0,75 \cdot 10\mu s = 7,5\mu s$$

$$\Delta I_L = \frac{U_{be} t_{be}}{L} \Rightarrow L = \frac{U_{be} t_{be}}{\Delta I_L} = \frac{12 \cdot 7,5\mu s}{5} = 18\mu H \quad (1p)$$


$$\Delta U_{ki} = \frac{I_{ki} t_{be}}{C} \Rightarrow C = \frac{I_{ki} t_{be}}{\Delta U_{ki}} = \frac{5 \cdot 7,5\mu s}{0,01} = 3750\mu F \quad (1p)$$

c.

$$\hat{I}_{ki} = \hat{I}_D = I_{LAV} + \frac{\Delta I_L}{2} = \frac{1}{1-d} I_{ki} + \frac{\Delta I_L}{2} = \frac{1}{1-0,75} \cdot 5 + \frac{5}{2} = 22,5A \quad (1p)$$

d.
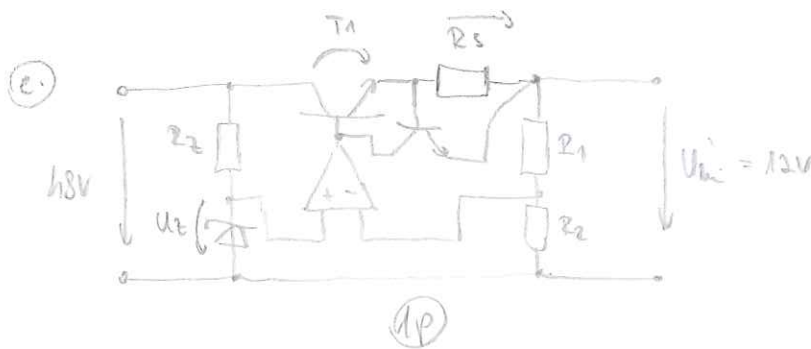
$$U_{ki} = U_D = U_{ki} = 48V \quad (1p)$$



f.

$$U_z = 5V$$

$$\frac{18V - 5V}{I_{zmax}} = \frac{18V - 5V}{0,5mA} = 86k\Omega > R_z > \frac{18V - 5V}{10mA} = 1,3k\Omega \quad (R_z = 10k\Omega) \quad (1p)$$

$$U_{ki} \cdot \frac{R_2}{R_1 + R_2} = U_z \Rightarrow U_{ki} = U_z \cdot \frac{R_1 + R_2}{R_2} \Rightarrow \frac{R_1 + R_2}{R_2} = 2,4$$

g.

$$R_1 + R_2 > \frac{12V}{1mA} = 12k\Omega$$

$$R_1 = 1,4 R_2$$

$$\left. \begin{array}{l} R_1 + R_2 > 12k\Omega \\ R_1 = 1,4 R_2 \end{array} \right\} \begin{array}{l} R_2 = 10k\Omega \\ R_1 = 14k\Omega \end{array} \quad (1p)$$

h.

$$I_{kcalid} = \frac{U_{be}}{R_s} \Rightarrow R_s \approx \frac{0,7V}{0,25A} = 2,8\Omega \quad (1p)$$

i.

$$P_D \approx P_{T1} + I_{ki}^2 R_s = (U_{be} - (U_{ki} + I_{ki} R_s)) \cdot I_{ki} + I_{ki}^2 R_s = (12 - (48 + 0,25 \cdot 2,8)) \cdot 0,25 + 0,25^2 \cdot 2,8$$

$$= 8,825 + 0,175 = 9W \quad (1p)$$

$$I_{DCDC} = 0,25A$$

$$I_{LAV} = \frac{1}{1-d} I_{DC} = 1 \cdot 0,25 = 1A \quad \Delta I_L = 5A$$

↖
Sangat kecil untuk stabilisasi

$$U_{ki} = U_{be} \left(1 + \frac{U_{be} \cdot t_{be}^2}{2L I_{DC}} \right) = 12 \left(1 + \frac{12 \cdot (7,5 \cdot 10^{-6})^2}{2 \cdot 10 \cdot 10^{-6} \cdot 0,25} \right) = 102V \quad (1p)$$

$$I_2 = \frac{102V - 5V}{100\Omega} = 2,425mA \quad (1p)$$

$$P_D \approx (102V - 12V) \cdot 0,25A = 22,5W \quad (1p)$$

$$\leq 14p$$

Oscilloscope: 25 part

$$0 - 10 : 1$$

$$11 - 15 : 2$$

$$16 - 19 : 3$$

$$20 - 22 : 4$$

$$23 - 25 : 5$$